
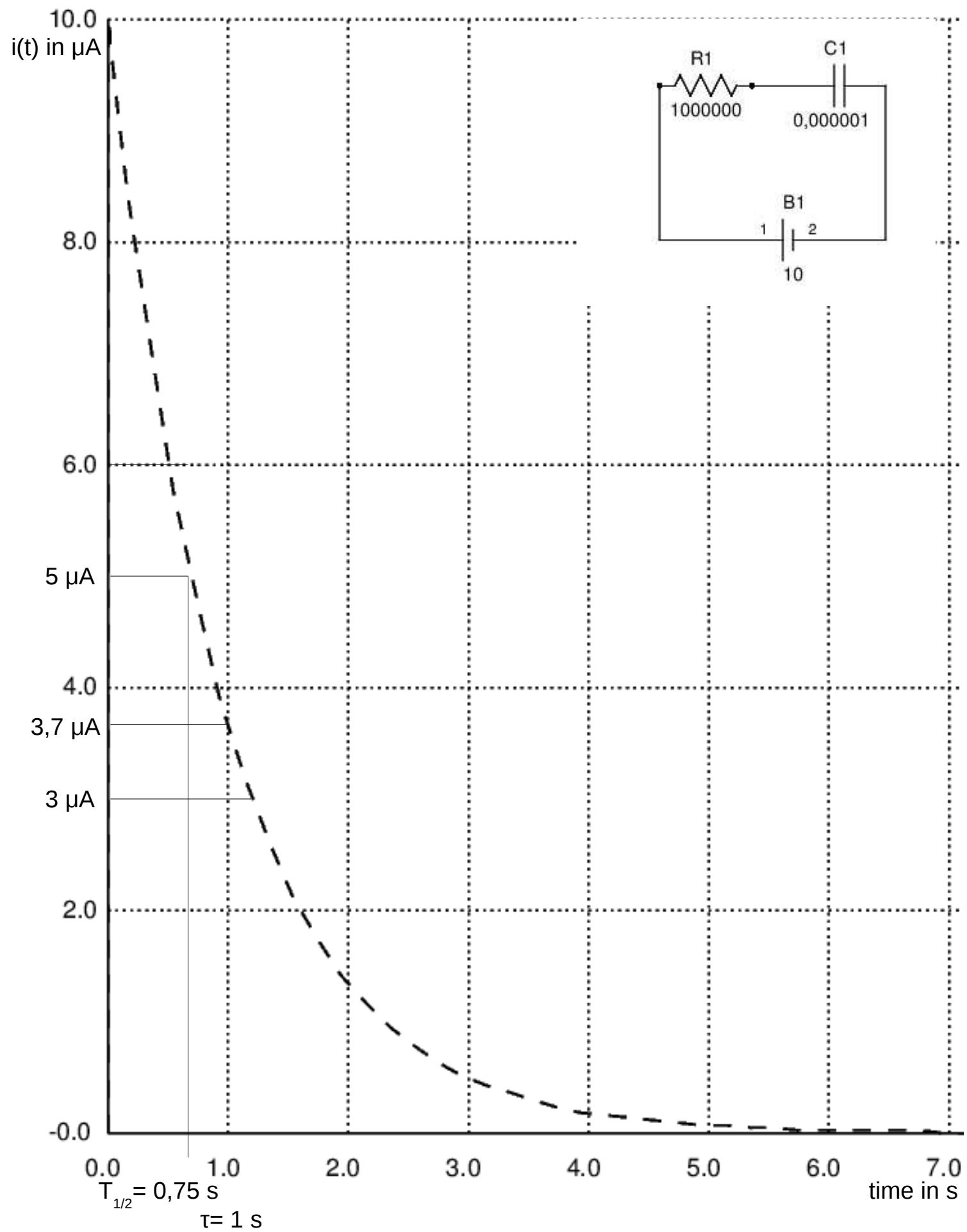


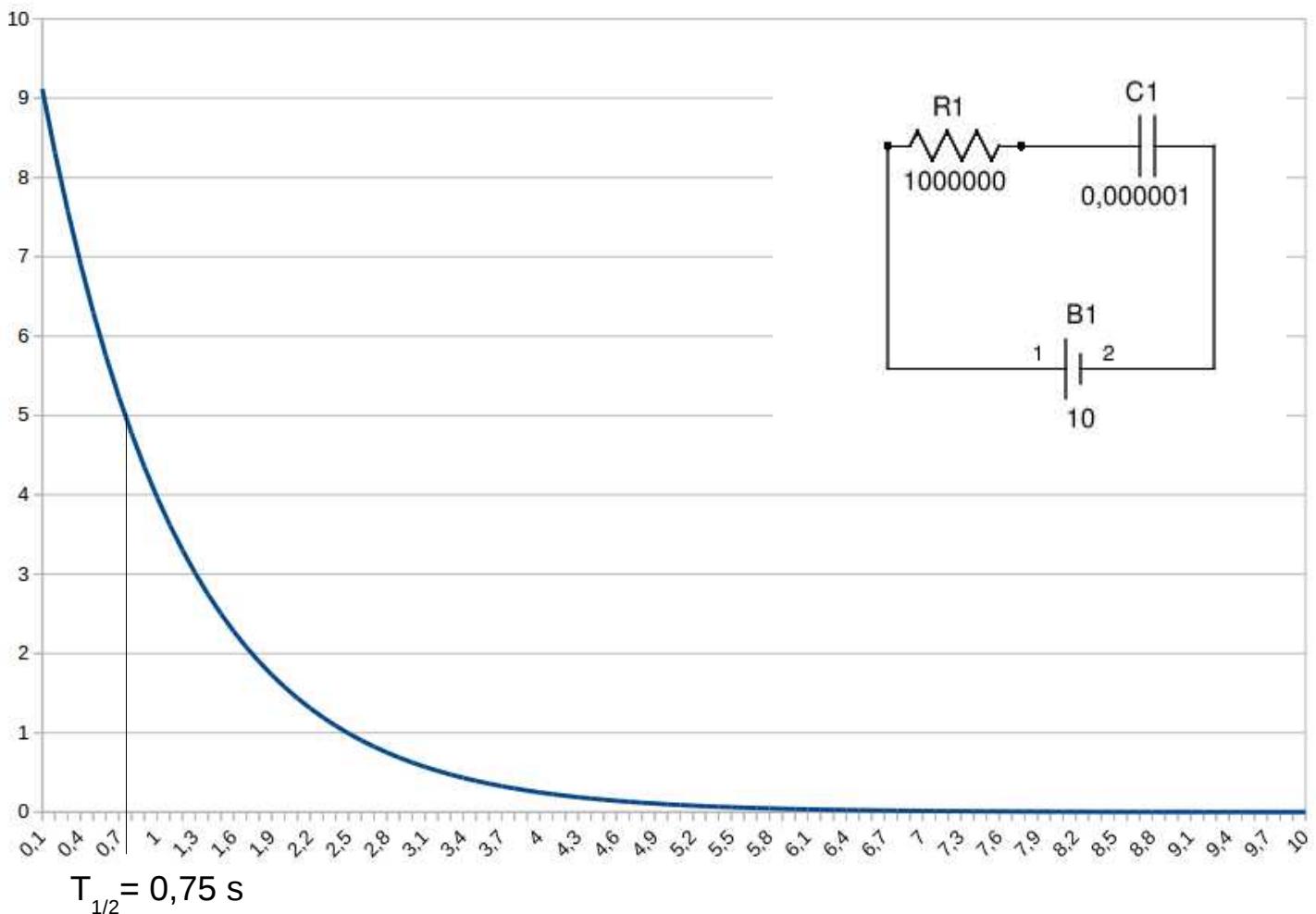Current in RC series circuit (10 V, 1 MΩ, 1 µF)
-> $\tau = RC = 1$ s mathematical solution



Calculation of $i(t)$ assuming a half-life period graphically determined of $T_{1/2} = 0,75$ s

$$10e-0924*t$$



The derivative of the function must be negative, since it's falling.

 The derivative is assumed to be proportional to the function's momentary value.



$$\begin{aligned} -\frac{di(t)}{dt} &= \lambda i(t) & \frac{di(t)}{i(t)} &= -\lambda dt & \int \frac{di(t)}{i(t)} &= \int -\lambda dt & \ln i(t) &= -\lambda t & i(t) &= e^{-\lambda t} \\ \frac{i(t)}{i(t+T_{1/2})} &= 2 = \frac{e^{-\lambda T_{1/2}}}{e^{-\lambda(t+T_{1/2})}} & 2 = e^{\lambda T_{1/2}} \rightarrow \lambda &= \frac{\ln 2}{T_{1/2}} & \text{with } T_{1/2} &= 0,75 \text{ s} \rightarrow \lambda &= 0,924 \end{aligned}$$

$$i(t) = i_0 \cdot e^{-\lambda t} \quad \lambda = \frac{1}{\tau} \rightarrow \frac{i(\tau)}{i_0} = e^{-1} = 0,37$$

Graphical solution for $i = 3,7 \mu\text{A} \rightarrow \tau = 1\text{s}$

$$i_C(t) = C \cdot \frac{du(t)}{dt} \rightarrow R \cdot i_C(t) = RC \cdot \frac{du(t)}{dt} \quad u_R(t) = RC \cdot \frac{du(t)}{dt} \rightarrow \frac{dt}{RC} = \frac{du(t)}{u_R(t)} \rightarrow \int \frac{dt}{RC} = \int \frac{du(t)}{u_R(t)}$$
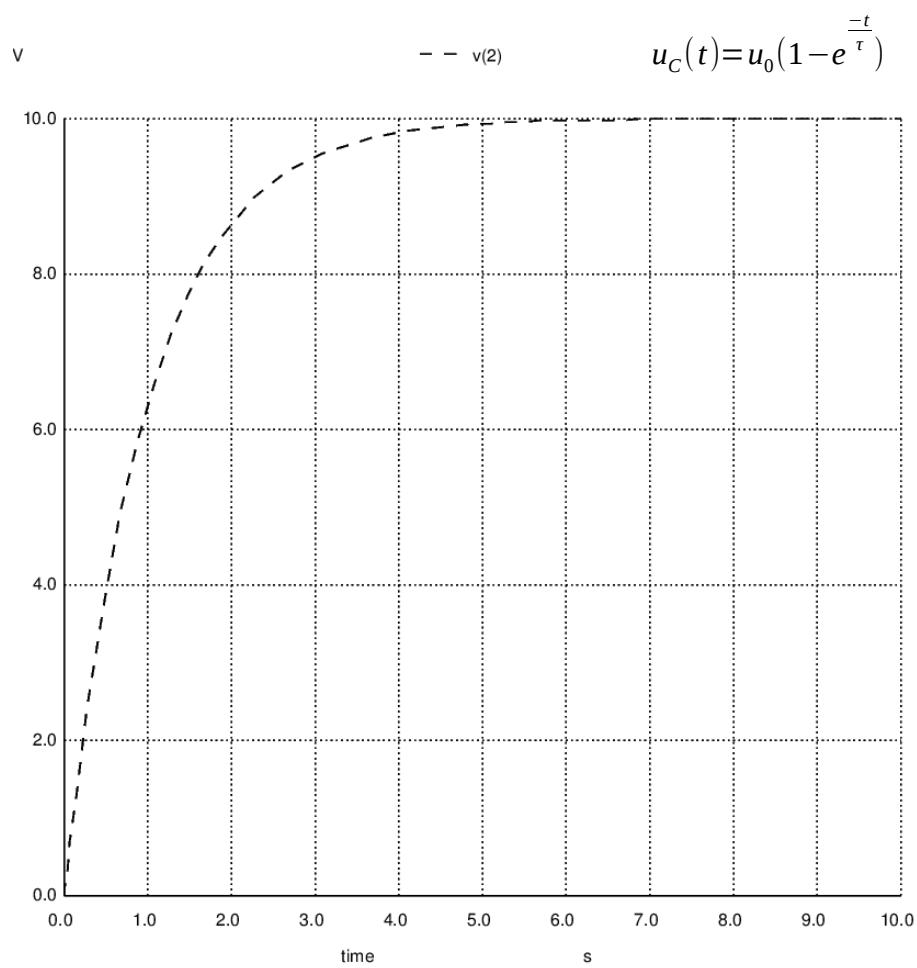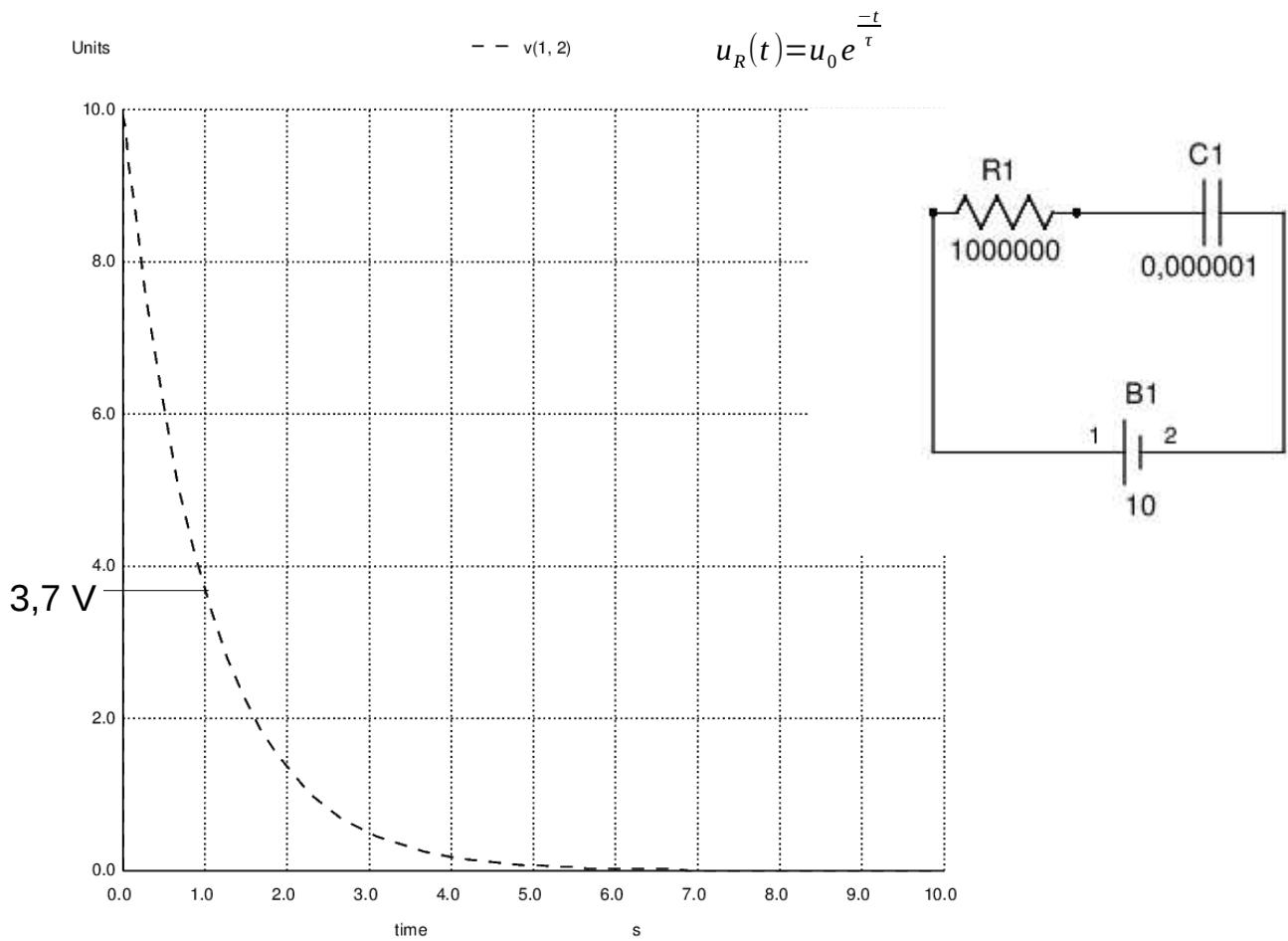
$$\frac{t}{RC} = \ln u_R(t) \quad \text{--- for } t = RC \quad \rightarrow \ln u_R(RC) = 1 \rightarrow u_R(RC) = e^1$$



NGSPICE NETLIST

***1 uF -- 1 Mohm ***

*V1 = 0V (initial value), V2 = 10V (pulsed value), TD = 0s (delay time), TR = 2ns (rise time), TF = 2ns (fall time),

*PW = 10s (pulse width)

vin 1 0 PULSE(0 10 0 2NS 2NS 10)

*resistor, the first 2 numbers are the nodes, the third the resistance value in Megaohm
r1 1 2 1Meg

*capacitor, the first 2 numbers are the nodes, the third the resistance value in uF

c1 2 0 1u

.control

tran .5s 10s; transient analysis

plot -vin#branch; i(t)

plot v(1, 2); vR(t)

plot v(2); vC(t)

.endc

.end